

# Hardware Assignment

## AI1110: Probability and Random Variables

### Indian Institute of Technology Hyderabad

Dudekula Dheeraj  
CS22BTECH11019

Random number generators using shift registers

#### COMPONENTS:

| Component             | Value        | Quantity |
|-----------------------|--------------|----------|
| Breadboard            |              | 1        |
| Seven Segment Display | Common Anode | 1        |
| Decoder               | 7447         | 1        |
| Flip Flop             | 7474         | 2        |
| X-OR Gate             | 7486         | 1        |
| 555 IC                |              | 1        |
| Resistor              | 1 K $\Omega$ | 1        |
| Capacitor             | 100 nF       | 1        |
| Capacitor             | 10 nF        | 1        |
| Jumper Wires          |              |          |

#### WORKING PROCEDURE

- 1) Connect the 555 timer circuit as shown in fig1. Then the clock signal output is generated.
- 2) The output generated is connected to 3rd and 11th pins of both 7474 IC's. These 7474IC's contains 2 D-flip flops inside them. It is shown in fig2.
- 3) The output of 1st and 4th flipflop is connected to input of XOR gate(7486) as in fig 3 and output of XOR is connected to input of 1st flip flop.
- 4) Connect the Decoder's(7447) A, B, C, D with output of each flip flops( $Q_0$ ,  $Q_1$ ,  $Q_2$ ,  $Q_3$ ) decoder is shown in fig4.
- 5) Then connect the 7-segment display with the decoder. refer fig-5 and fig-6.

#### OUTPUT

7-segment display displays a random number from 0 – 9.

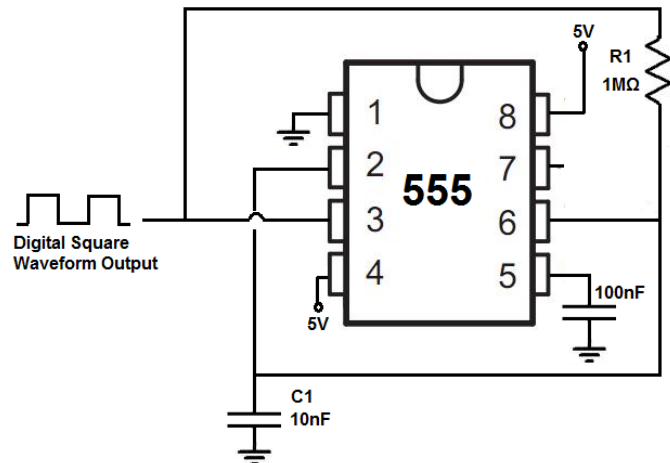


Fig. 1. 555 timer circuit

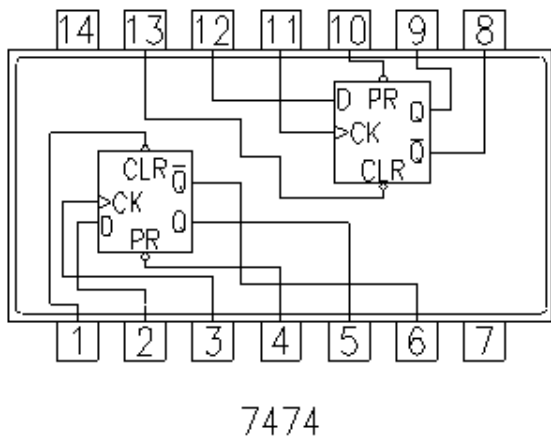


Fig. 2. 7474 containing 2 D-Flipflops

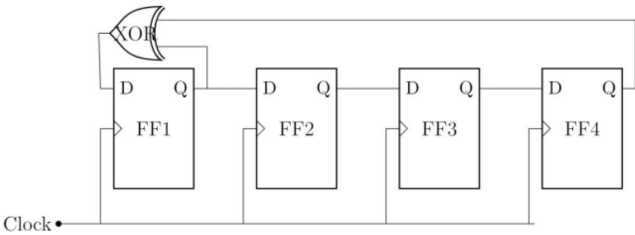


Fig. 3. connections between two 7474's and 7486



Fig. 4. Decoder 7447

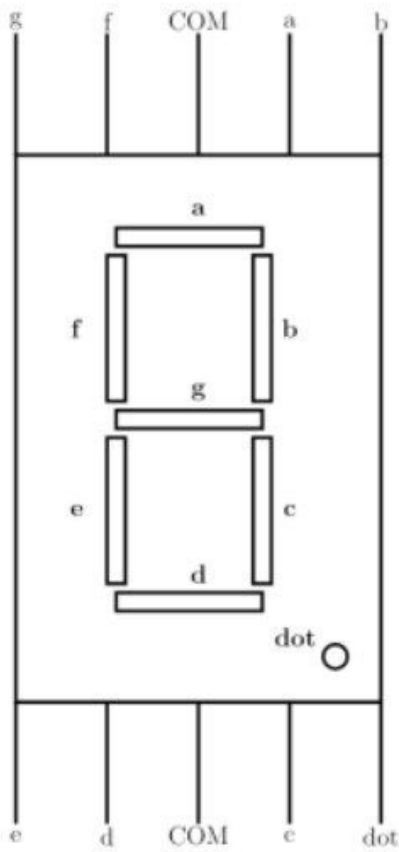


Fig. 5. 7 segment display

| 7447    | $\bar{a}$ | $\bar{b}$ | $\bar{c}$ | $\bar{d}$ | $\bar{e}$ | $\bar{f}$ | $\bar{g}$ |
|---------|-----------|-----------|-----------|-----------|-----------|-----------|-----------|
| Display | a         | b         | c         | d         | e         | f         | g         |

Fig. 6. table

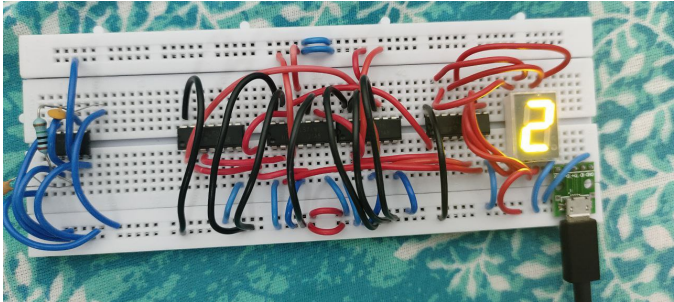


Fig. 7. output