

# Hardware Assignment

## AI1110: Probability and Random Variables

### Indian Institute of Technology Hyderabad

Arugonda Srikar  
CS22BTECH11008

### Random number generators using shift registers

#### COMPONENTS:

Component	Value	Quantity
Breadboard		1
Seven Segment Display	Common Anode	1
Decoder	7447	1
Flip Flop	7474	2
X-OR Gate	7486	1
555 IC		1
Resistor	1 K $\Omega$	1
Capacitor	100 nF	1
Capacitor	10 nF	1
Jumper Wires		

#### WORKING PROCEDURE

- 1) Connect the 555 timer circuit as shown in fig1. Then the clock signal output is generated.
- 2) The output generated is connected to 3rd and 11th pins of both 7474 IC's. These 7474IC's contains 2 D-flip flops inside them. It is shown in fig2.
- 3) The output of 1st and 4th flipflop is connected to input of XOR gate(7486) as in fig 3 and output of XOR is connected to input of 1st flip flop.
- 4) Connect the Decoder's(7447) A, B, C, D with output of each flip flops( $Q_0$ ,  $Q_1$ ,  $Q_2$ ,  $Q_3$ ) decoder is shown in fig4.
- 5) Then connect the 7-segment display with the decoder. refer fig-5 and fig-6.

#### OUTPUT

7-segment display displays a random number from 0 – 9.

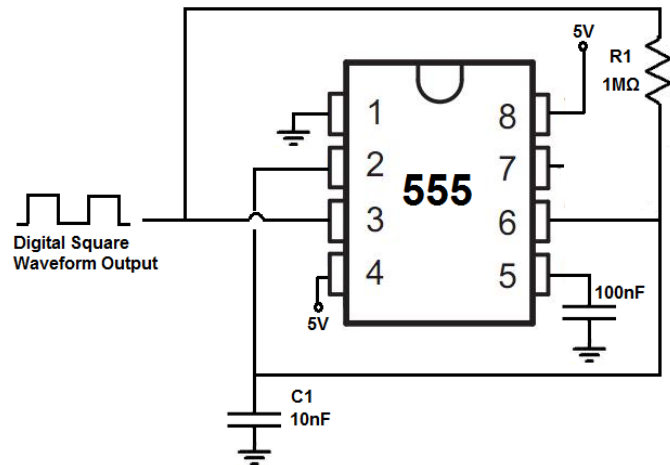


Fig. 1. 555 timer circuit

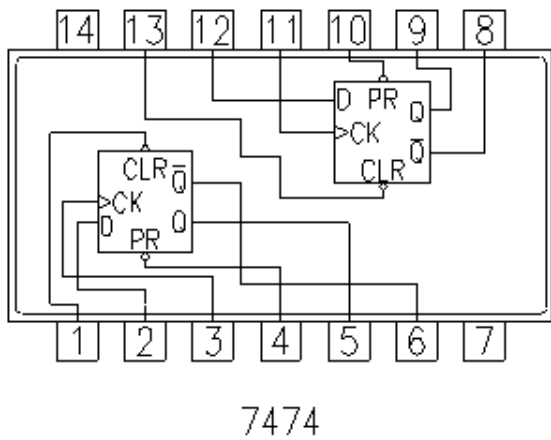


Fig. 2. 7474 containing 2 D-Flipflops

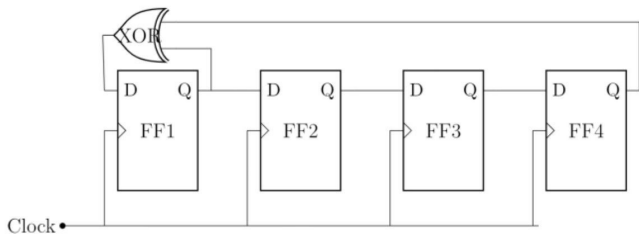


Fig. 3. connections between two 7474's and 7486

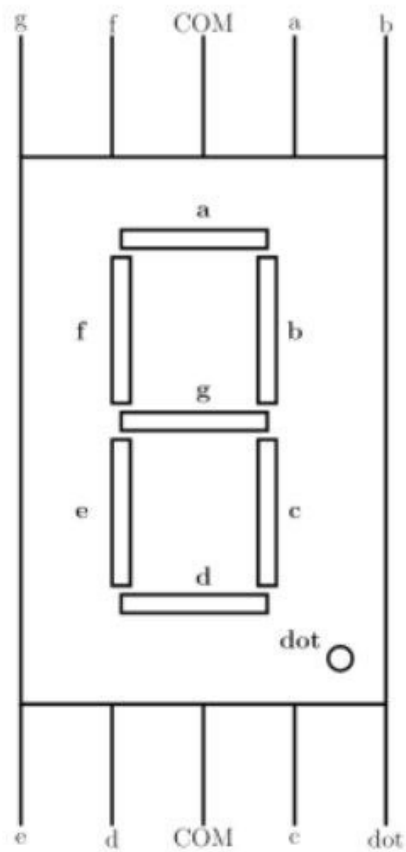


Fig. 5. 7 segment display

7447	$\bar{a}$	$\bar{b}$	$\bar{c}$	$\bar{d}$	$\bar{e}$	$\bar{f}$	$\bar{g}$
Display	a	b	c	d	e	f	g

Fig. 6. table



Fig. 4. Decoder 7447

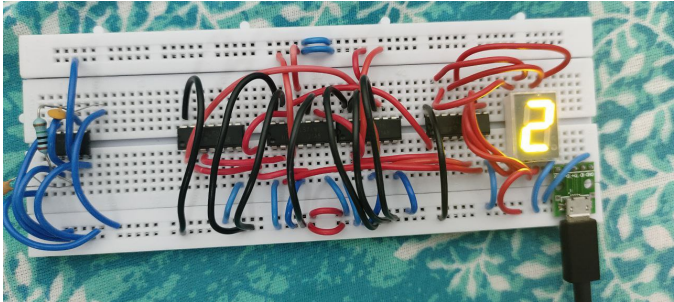


Fig. 7. output